

Circuits and Circuit Elements

Problem D**CURRENT IN AND POTENTIAL DIFFERENCE ACROSS A RESISTOR PROBLEM**

Determine the current in and the potential difference across the $5.0\ \Omega$ resistor in the circuit diagram at right.

SOLUTION


1. **Determine the equivalent resistance in the circuit.**

For group (a): $R_{eq,a} = 5.0\ \Omega + 2.0\ \Omega = 7.0\ \Omega = R_2$

$$\text{For group (b): } \frac{1}{R_{eq,b}} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{4.0\ \Omega} + \frac{1}{7.0\ \Omega}$$

$$\frac{1}{R_{eq,b}} = \frac{0.25}{1\ \Omega} + \frac{0.14}{1\ \Omega} = \frac{0.39}{1\ \Omega}$$

$$R_{eq,b} = 2.6\ \Omega$$

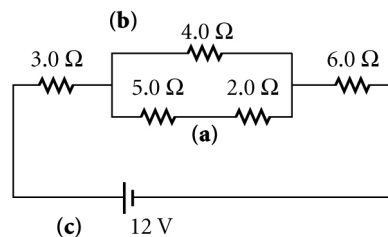

For group (c): $R_{eq,c} = 3.0\ \Omega + 2.6\ \Omega + 6.0\ \Omega = 11.6\ \Omega$

2. **Calculate the total current in the circuit, which is the current in group (c).**

$$I = \frac{\Delta V_{tot}}{R_{eq}} = \frac{12.0\ \text{V}}{11.6\ \Omega} = 1.0\ \text{A}$$

3. **Determine a path from the equivalent resistance found in step 1 to the $5.0\ \Omega$ resistor.** Review the path taken to find the equivalent resistance and work backward through this path.
4. **Follow the path determined in step 3, and calculate the current in and the potential difference across each equivalent resistance.** Repeat this process until the desired values are found.

Regroup, evaluate, and calculate. The circuit's equivalent resistance is that of group (c), as found in step 1 above. The resistors in group (c) are in series; therefore, the current in each resistor is the same as the current in the equivalent resistance, which equals 1.0 A. The potential difference across group (b), which is represented by the $2.6\ \Omega$ resistor in group (c), can be replaced with $\Delta V = IR$.

Given: $I = 1.0\ \text{A}$ $R = 2.6\ \Omega$

Unknown: $\Delta V = ?$

$$\Delta V = IR = (1.0\ \text{A})(2.6\ \Omega) = 2.6\ \text{V}$$

Regroup, evaluate, and calculate. Replace the center resistor with group (b). The resistors in group (b) are in parallel; therefore, the potential difference across each resistor is the same as the potential difference across the $2.6\ \Omega$ equivalent resistance, which equals 2.6 V. The current in the $7.0\ \Omega$ resistor in group (b) can be calculated using $I = \Delta V/R$.

Given: $\Delta V = 2.6 \text{ V}$ $R = 7.0 \Omega$

Unknown: $I = ?$

$$I = \frac{\Delta V}{R} = \frac{2.6 \text{ V}}{7.0 \Omega} = 0.37 \text{ A}$$

Regroup, evaluate, and calculate. Replace the 7.0Ω resistor with group (a). The resistors in group (a) are in series; therefore, the current in each resistor is the same as the current in the 7.0Ω equivalent resistance, which equals 0.37 A .

$$I = 0.37 \text{ A}$$

The potential difference across the 5.0Ω resistor can be calculated using

$$\Delta V = IR.$$

Given: $I = 0.37 \text{ A}$ $R = 5.0 \Omega$


Unknown: $\Delta V = ?$

$$\Delta V = IR = (0.37 \text{ A})(5.0 \Omega) = 1.85 \text{ V}$$


$$\Delta V = 1.85 \text{ V}$$

ADDITIONAL PRACTICE

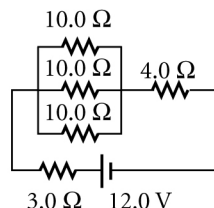
1. Determine the current in and the potential difference across the 4.0Ω resistor in the circuit diagram at right.



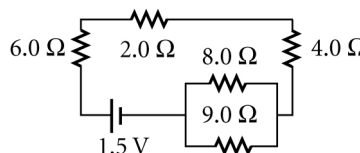
2. Determine the current in and the potential difference across the 9.0Ω resistor in the circuit diagram at right.



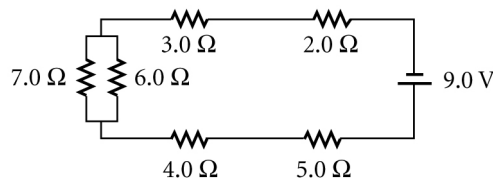
3. Determine the current in and the potential difference across the 6.0Ω resistor in the circuit diagram at right.



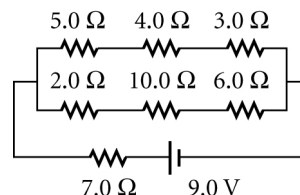
4. Determine the current in and the potential difference across the 10.0Ω resistor in the circuit diagram at right.



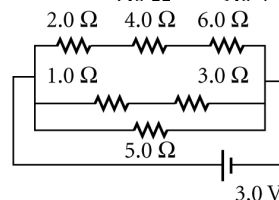
5. Determine the current in and the potential difference across the 4.0Ω resistor in the circuit diagram at right.



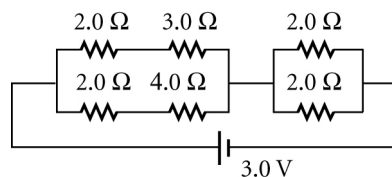
6. Determine the current in and the potential difference across the $3.0\ \Omega$ resistor in the circuit diagram at right.



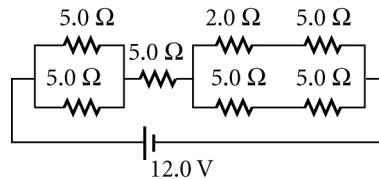
7. Determine the current in and the potential difference across the $2.0\ \Omega$ resistor in the circuit diagram at right.



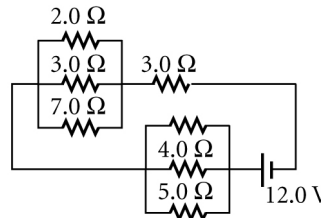8. Determine the current in and the potential difference across the $7.0\ \Omega$ resistor in the circuit diagram at right.



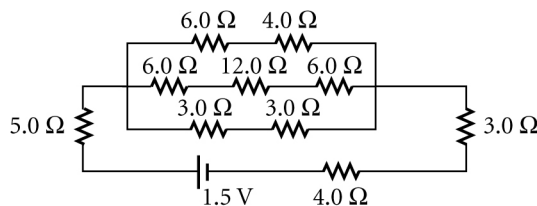9. Determine the current in and the potential difference across the $12.0\ \Omega$ resistor in the circuit diagram at right.



10. Determine the current in and the potential difference across the $15.0\ \Omega$ resistor in the circuit diagram at right.

