

Name: \_\_\_\_\_

Word bank: Adds, Constant, One, More than One, Reciprocals Add to give the Reciprocal

## Characteristics of Series and Parallel Circuits

	<b>Series</b>	<b>Parallel</b>
<b>Number of Paths</b>		
<b>Current</b>		
<b>Voltage</b>		
<b>Resistance</b>		
<b>Power</b>		

Name: \_\_\_\_\_

Word bank: Adds, Constant, One, More than One, Reciprocals Add to give the Reciprocal

## Characteristics of Series and Parallel Circuits

	<b>Series</b>	<b>Parallel</b>
<b>Number of Paths</b>		
<b>Current</b>		
<b>Voltage</b>		
<b>Resistance</b>		
<b>Power</b>		